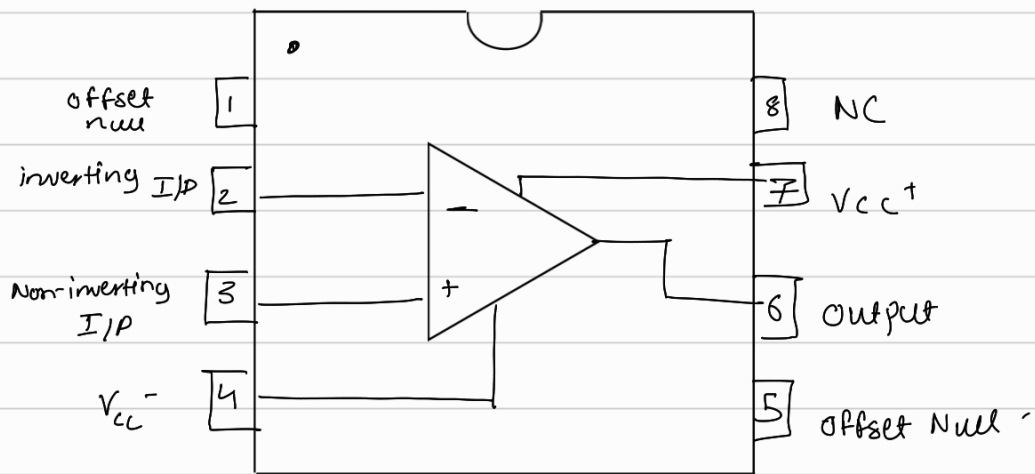


OP AMP (741 IC)




use pins: 2, 3, 4, 6, 7

check with all inputs (Differentiator)

sine, triangular, square.

Waveform	I/P	O/P
	$V_{pp}(V)$ $f(KHz)$	$V_{pp}(V)$ $f(KHz)$

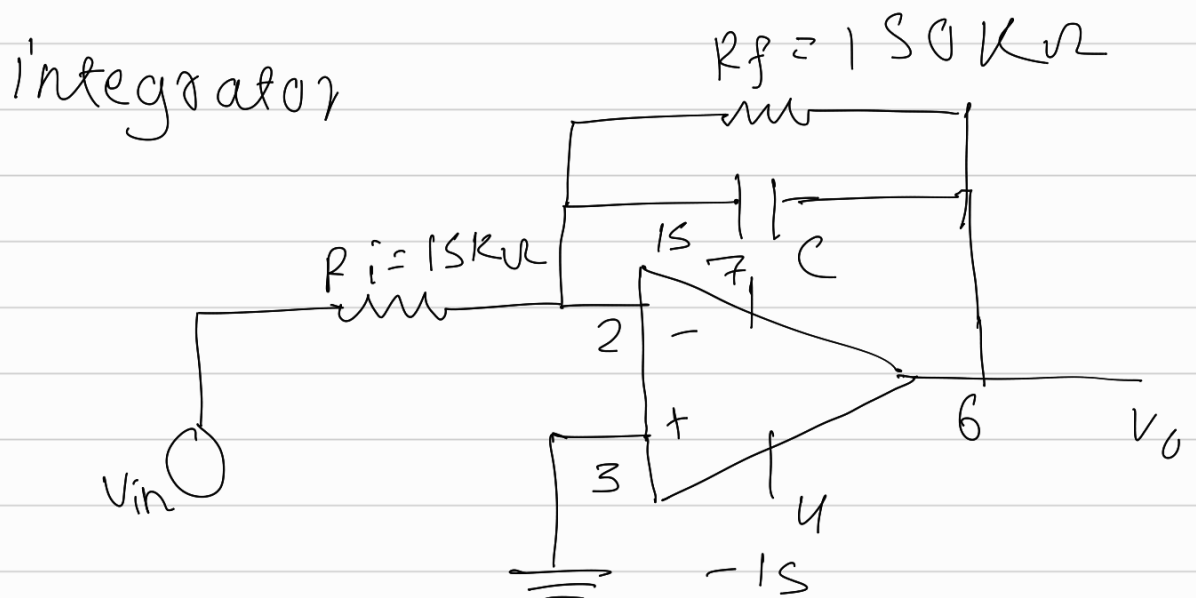

Objective

Software used

circuit diagram & theory

procedure

observations

wave form

Results.

wave form	I/P		O/P	
	$V_{pp}(V)$	$f(KHz)$	$V_{pp}(V)$	$f(KHz)$
Sine	10.2V	34 KHz	12.4V	34 KHz
Sqr	10.2V	"	10.4V	"
tri	9.8V	"	9.8V	"
differ				
Sine				
Sqr	5.12		9.40	
tri	5.04		3.28	