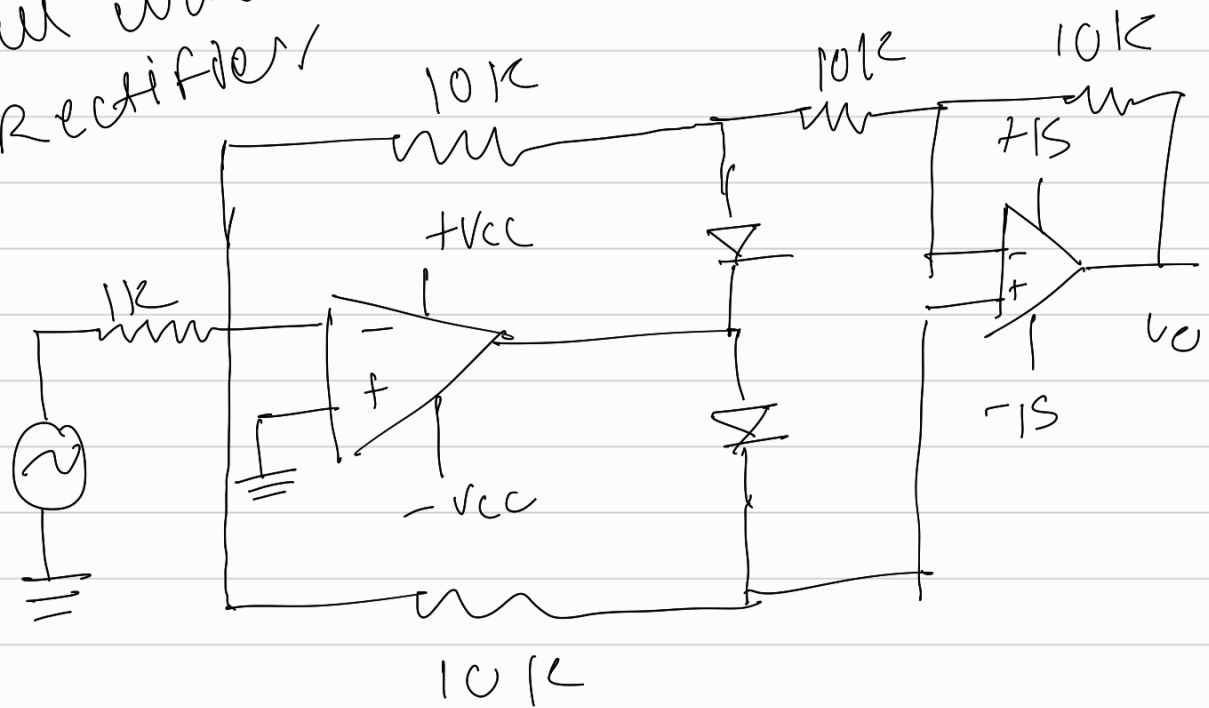


Full wave Rectifier



$$\text{Theory} = A_v = \frac{V_o}{V_{in}} = -\frac{R_f}{R_{in}}$$

$$= \frac{10k}{1k} = 10$$

$$\text{Practical} = \frac{V_o}{V_{in}} = \frac{9.8}{1} = 9.8$$