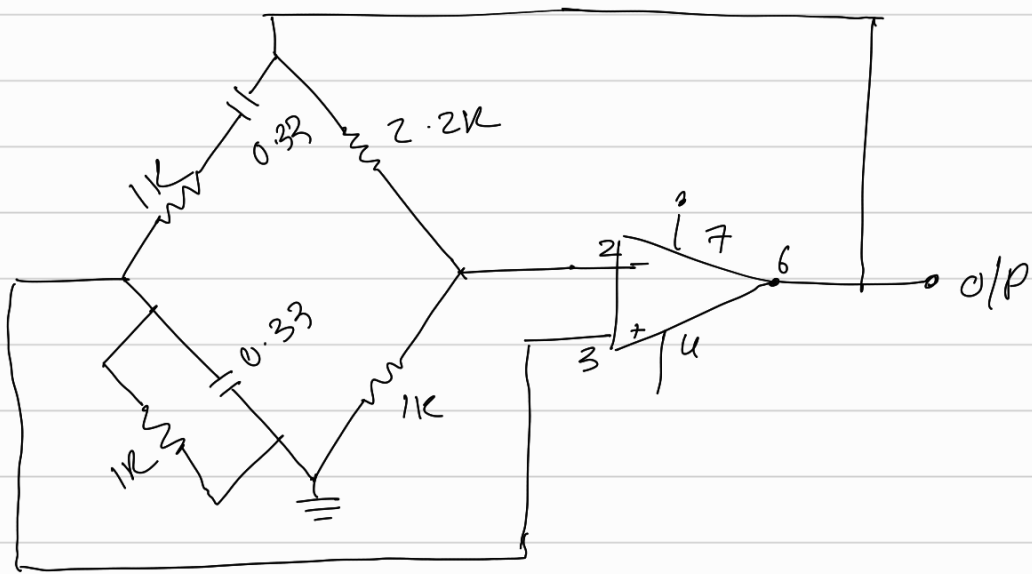


Wien Bridge Oscillation



Practical

469Hz

Theoretical

$$\frac{1}{2\pi RC} = 482\text{Hz}$$