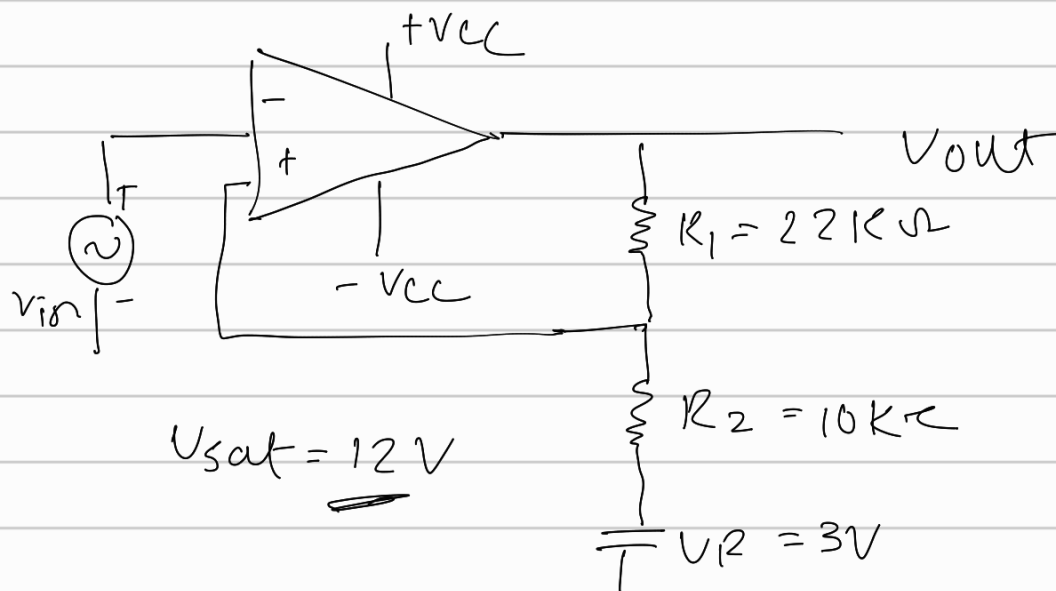


objective: Design and verify schmitt trigger



$$V = V_{UTP} - V_{LTP}$$

$$V_{UTP} = \frac{V_{ref} R_1}{R_1 + R_2} + \frac{V_{sat} R_1}{R_1 + R_2} = 1.375 + 8.25 = 9.625$$

$$V_{LTP} = \frac{V_{ref} R_1}{R_1 + R_2} - \frac{V_{sat} R_1}{R_1 + R_2} = 1.375 - 8.25 = -6.875$$

UTP

LTP

theory prac theory prac

9.625 2.96 -6.875 -2.08

