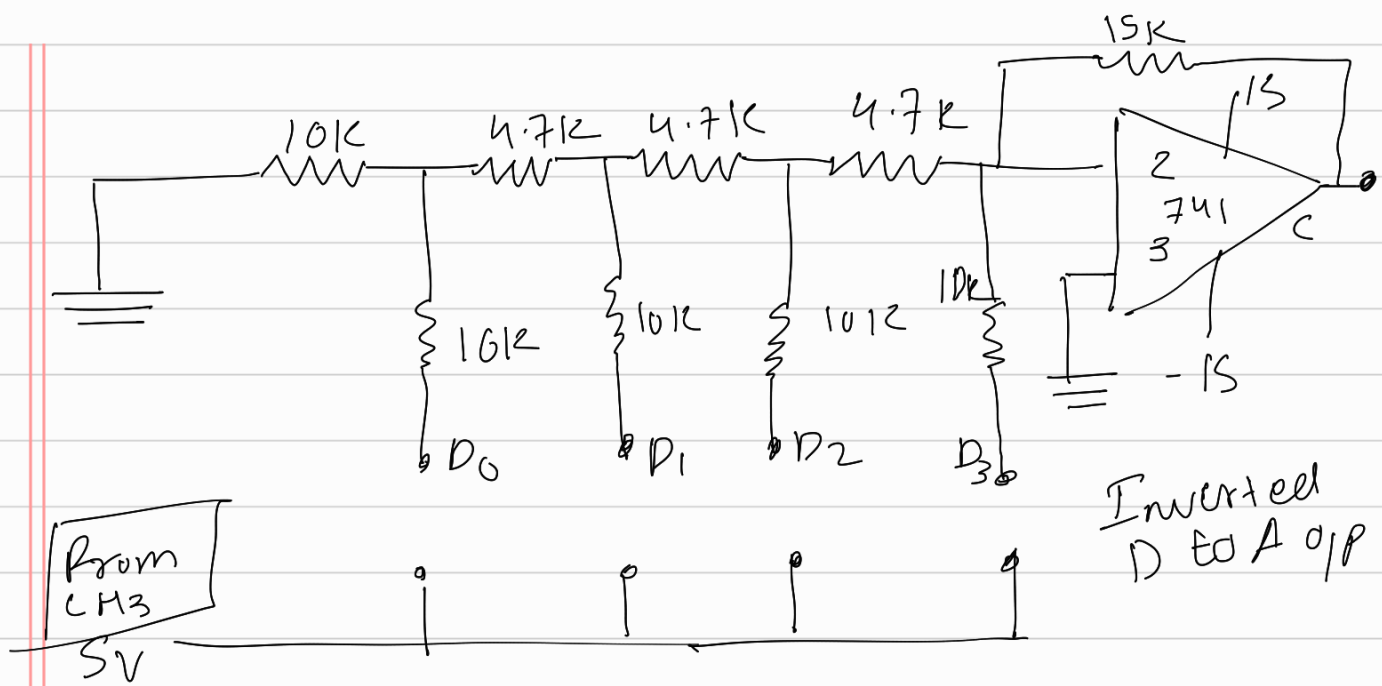




$D_0 - D_3$ connect either
5V or Gnd.

D_3	D_2	D_1	D_0	O/P
0	0	0	0	0.02
0	0	0	1	-1.003
0	0	1	0	-1.943
0	0	1	1	-2.947
0	1	0	0	-3.869
0	1	0	1	-4.973
0	1	1	1	-5.812
1	0	0	0	-6.68